

2022

Time - 3 hours

Full Marks - 60

*Answer all groups as per instructions.
Figures in the right hand margin indicate marks.
Candidates are required to answer
in their own words as far as practicable.*

GROUP – A

1. Fill in the blanks. (all)

[1 × 8

(a) Transistor is a/an _____ component.

(b) $(11001)_2 = (\text{_____})_{10}$.

(c) $(3F9)_{16} = (\text{_____})_{10}$.

(d) Decimal number $(2157)_{10}$ in BCD is _____.

(e) $A + 1 = \text{_____}$

(f) $A + A' = \text{_____}$

(g) In a cathode ray oscilloscope, electrons are produced by _____.

(h) OR logic gates can be realized by two _____ biased diodes.

P.T.O.

[2]

GROUP – B

2. Answer any eight of the following questions within two to three sentences each. [1½ × 8

- (a) Write two advantages of ICs.
- (b) What is aquadag ? What is its role in CRO ?
- (c) What is 555 IC ? Give two of its important features.
- (d) What do you mean by Shift Register ? Why is it named so ?
- (e) Write the basic differences between 4 bit synchronous up and down counters.
- (f) What is the function of input of a computer ?
- (g) Add BCD numbers 0111 and 0101.
- (h) What are Active and Passive components ?
- (i) What is BCD ?
- (j) What is ROM ?

GROUP – C

3. Answer any eight of the following questions within 75 words each. [2 × 8

- (a) Explain why the transistor is an active device.
- (b) What are the differences between analog and digital signals ?

[3]

- (c) Convert $(AB12)_{16}$ into octal number.
- (d) State and prove De Morgan's first theorem.
- (e) Find the 1's complement of -7 .
- (f) What is RAM ? What are the basic types of RAM ?
- (g) What is electrostatic deflection sensitivity ?
- (h) What are the advantages and limitations of ICs ?
- (i) What is an IC chip ?
- (j) Convert $(30.524)_{10}$ into binary.

GROUP – D

Answer any four questions within 500 words each.

- 4. Explain the different classifications of ICs. What are the advantages and limitations ? [6]
- 5. What is a Chip ? Explain the various steps required in the production of IC. [6]
- 6. Explain the working of an OR gate and an AND gate using diodes and transistor circuit. [6]
- 7. Show that the NAND gate and NOR gate can be used as universal gates. [6]

P.T.O.

[4]

8. Discuss about a half adder and full adder of digital circuit. [6]
9. Discuss about a half subtractor and full subtractor of digital circuit. [6]
10. What is a shift register ? Discuss about a 4-bit serial in parallel out shift register. [6]
11. Discuss about a 4-bit synchronous decade counter. [6]