

2020-21
Time - 3 hours
Full Marks – 60

*Answer all groups as per instructions.
Figures in the right hand margin indicate marks.
Candidates are required to answer
in their own words as far as practicable.*

Group-A

1. Answer all questions. [1x8]
- a) The temperature coefficient of resistance of semiconductor is_____.
 - b) The potential difference across the depletion region is known as _____ potential.
 - c) A Zener diode is always _____ biased.
 - d) Define cut off point.
 - e) Which type of feedback in amplifier reduces output noise?
 - f) The LED is _____ power device.
 - g) An oscillator is _____ converter.
 - h) The average input signal is known as _____ signal.

Group-B

2. Answer any eight of the following questions within two or three sentences each. [$1\frac{1}{2}$ x8]
- a) What is step junction?
 - b) Find the reactance of capacitor to the direct current.
 - c) What is ripple factor?
 - d) Draw the wave form of Input A.C. voltage and output D.C. voltage for a full wave rectifier.
 - e) Find value of α if $\beta = \gamma = 20$.
 - f) Find emitter current in a transistor if $\beta = 60$ and $I_b = 20$ mA.

- g) Name the different methods of biasing a transistor.
- h) The gain of an amplifier is 200. If positive feedback is applied, gain increases to 500. Find the feedback fraction.
- i) Determine the frequency of oscillation in an LC oscillator circuit if $L = 60 \mu\text{H}$ and $c = 200 \text{ PF}$.
- j) What is an inverter?

GROUP-C

3. Write notes on any eight of the followings within 75 words: [2x8]

- a) Explain the mechanism of current conduction in p-type semiconductor.
- b) Find static resistance of a junction diode if 50 mA current flows through it for a forward voltage 2 V at 300 K.
- c) Find output DC voltage, if an input A.C. voltage 220 V is applied to a half wave rectifier through a transformer of transformer ratio 0.4.
- d) What is Zener diode? Draw the equivalent circuit of an ideal Zener diode.
- e) Establish the relation

$$I_c = \alpha I_E + I_{CBO} \text{ for CB connection of transistor.}$$

- f) Find zero signal value of I_c for a germanium transistor with $\beta=50$ and $R_B=250 \text{ k}\Omega$ in fixed bias method, Given $V_{cc} = 12 \text{ V}$.
- g) Discuss the advantages and disadvantages of RC coupled amplifier.
- h) Prove that negative feedback improves the stability of gain.
- i) Discuss the frequency response of an operational amplifier.

GROUP- D

4. Answer any four questions within 500 words each. [6x4]

- a) What is LED? Explain the working of LED. Discuss the applications of LED.
- b) Derive expression for barrier potential for a step junction.

- c) Draw CE output characteristic and D.C. load line of a transistor
Explain saturation point, cut off point and active region in CE output characteristic.
- d) Discuss about construction and working of RC coupled two stage transistor amplifier.
- e) Explain with the help of block diagram, the working of negative voltage series feedback amplifier. Discuss how negative feedback increases circuit stability.
- f) With a neat circuit diagram, explain the working of Hartley oscillator.
Derive the condition for sustained oscillation.
- g) Discuss the operation of OP-AMP as –
- i) Integrator
 - ii) Subtractor.
